
 Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [1]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Analog Electronic Circuits

Prof. Mor M. Peretz


The Center for Power Electronics and Mixed-Signal IC
Department of Electrical and Computer Engineering
Ben-Gurion University of the Negev, ISRAEL
 Emails: morp@bgu.ac.il
 Website: <http://www.ee.bgu.ac.il/~pemic>
<http://www.ee.bgu.ac.il/~analog>

 Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [2]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Electronics Training – ECE, BGU (circuits/VLSI track)

Electronics training "chain" (under the circuit/VLSI track)

- Undergraduate:
 - Intro. to Analog Circuits
 - Digital Circuits
 - **Analog Electronic Circuits – THIS COURSE (aka Analog IC)**
 - Intro. to VLSI
 - VLSI Design (aka mixed-signal IC design)
 - Switch-Mode Power Supplies (aka DCDC)
- Graduate:
 - Problems in Electronic circuits
 - Digital control of switch-mode systems

 Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [3]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY


Logistics

- Lecturer: Prof. Mor M. Peretz
- Course hours: Sundays, 14-17
- Office hours:
 - PEMIC Center, Building 64, Rm. 4 (ground level)
 - Wednesdays 14-15
- Course website:
 - <http://www.ee.bgu.ac.il/~analog>
 - Slides will be updated before class
 - Videos will be uploaded during the semester
- Grading:
 - 100% final Exam
 - ***Attendance is not mandatory but highly recommended


Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [4]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Analog Electronic Circuits
 Course background and motivation

- Analog (continuous-time) signals
 - Continuous flow of information
 - Data derived from signals parameters: shape, amplitude, frequency
 - In Digital the info is discrete and finite



truscottjewellers.co.uk



sapling-inc.com

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [5]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY


Analog Electronic Circuits
 Course background and motivation


- We live in an ANALOG world (still...)
- The digital Revolution:
 - Simple designs, compact, scalable, upgradable, communication, fast time-to-market
- Any link to the "real world" needs interface
 - Computers, Mobile, Audio, Video, Communication
- **\$\$\$ The bottom line \$\$\$**
 - Electronics hardware engineers, in particular mixed-signal (analog) are *top earners with longest prospect across the board of hi-tech industry*

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [6]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Integrated vs discrete circuits

Die micrograph

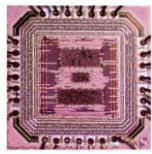

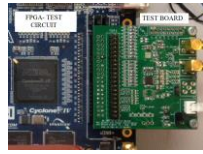

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [7]
THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Integrated vs discrete circuits

(a) (b)

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [8]
THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Recommended literature

- Course slides
- Sergio Franco, "Design With Operational Amplifiers And Analog Integrated Circuits" (any addition)
- Ramakant A. Gayakwad, "Op-amps and linear integrated circuit technology:
- David A. Johns, Ken Martin, "Analog Integrated Circuit Design"
- Hans Camenzind, "Designing Analog Chips"
- Analog IC Design - <http://www.aicdesign.org/>
- Analog Electronic circuits - <http://www.ee.bgu.ac.il/~angcirc>

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [9]
THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Lesson #1

Outline

- Review of basic transistor circuits
 - Current mirrors
 - Voltage reference (Bandgap)
 - Differential pair
- The operational amplifier (opamp)
 - Basic internal (transistor) circuit
 - Ideal amplifier
 - Characteristics of the ideal opamp
- Basic circuits
 - Inverting amp, Non-inverting amp
 - Summing, difference, integrator, differentiator
- Additional applications
 - Voltage reference, current source

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [10]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Current Mirror

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [11]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Voltage Reference (Bandgap)

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [12]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Differential Pair

$$I_{in} = I_{Q1} = \frac{V_{in}}{r_{o1} + r_{o2}} \quad r_x = 1/g_{m1}$$

$$Q_1 \text{ and } Q_2 \text{ have the same bias currents} \rightarrow g_{m1} = g_{m2}$$

$$I_{Q1} = \frac{g_{m1} V_{in}}{2} \quad I_{Q2} = I_{Q1} = -I_{Q1} \rightarrow I_{Q2} = -\frac{g_{m1} V_{in}}{2}$$

$$I_{out} = I_{Q1} - I_{Q2} \rightarrow I_{out} = g_{m1} V_{in}$$

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [13]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Differential Pair

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [14]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Differential Pair Two stages

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [15]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Three stages diff. pair – The Operational Amplifier

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [16]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

OpAmp characteristics

Ideal OpAmp primary features:

- Differential inputs
- Output product as function inputs $(V_+ - V_-) A$
 $A = A_1 A_2 A_3$
- Infinite gain $A \rightarrow \infty$
- Infinite Bandwidth $BW \rightarrow \infty$
- Infinite input resistance $R_{in} \rightarrow \infty$
- Zero output resistance $R_{out} \rightarrow 0$

V_{in}
 V_{out}
 $V_{out} = A(V_+ - V_-) A$

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [17]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Inverting Amp Virtual Ground

- Zero potential between inputs

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [18]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Non-inverting Amp

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [19]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Summing Amp

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [20]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Difference Amp

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [21]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Integrator Amp

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [22]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Differentiator Amp

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [23]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Voltage reference by OpAmp (Bandgap)

Prof. Mor M. Peretz Analog Electronic Circuits 361-1-3671 [24]
 THE CENTER FOR POWER ELECTRONICS AND MIXED-SIGNAL IC, BEN-GURION UNIVERSITY

Current source by OpAmp
